
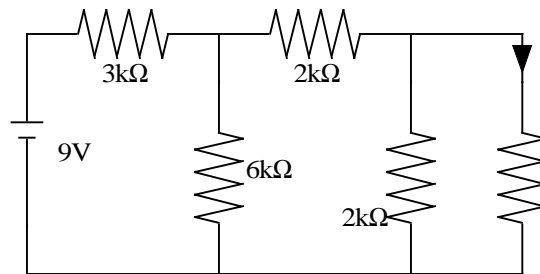

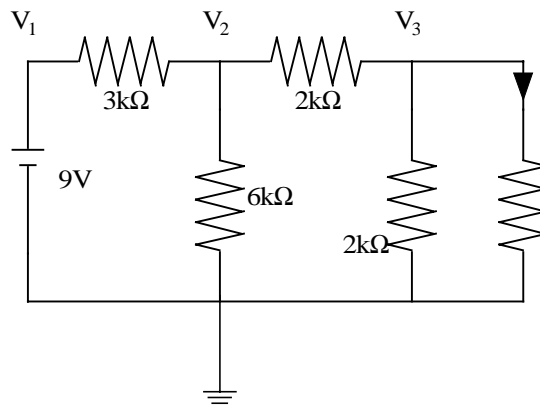
### Problem 3.5

Find  $I_0$  in the circuit using nodal analysis



### Suggested Solution



$$V_1 = 9V$$

$$\frac{9 - V_2}{3k} = \frac{V_2}{6k} + \frac{V_2 - V_3}{2k}$$


$$\frac{V_3 - V_2}{2k} + \frac{V_3}{2k} + \frac{V_3}{2k} = 0 \Rightarrow V_3 = 1.2V, I_0 = \frac{1.2}{2k} = 0.6mA$$

$$V_3 = 1.2V$$


$$I_0 = 0.6mA$$
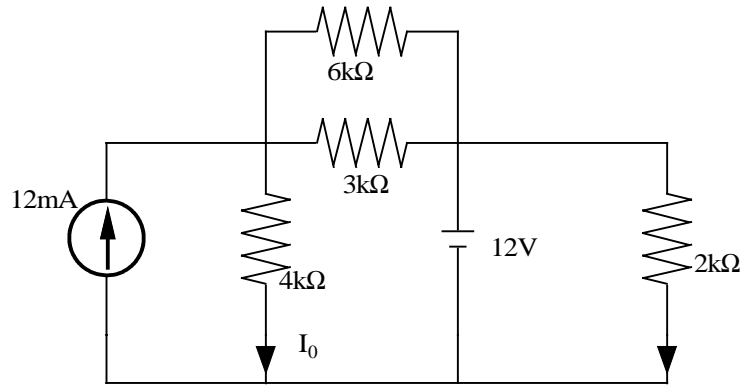
### Problem 3.10

Use nodal analysis to find out  $I_0$  and  $I_1$



**Suggested Solution**

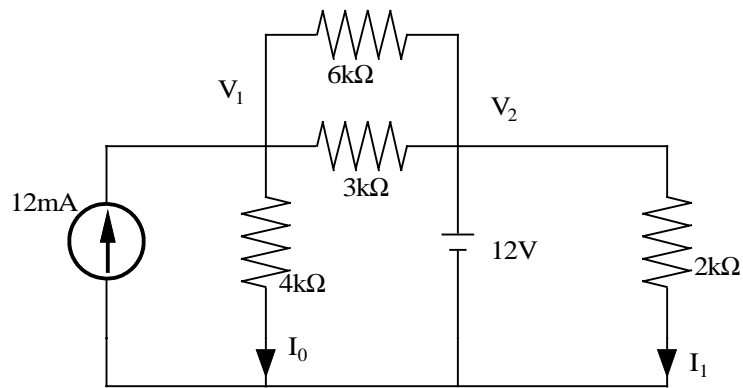

$$V_1 = -12V; I_1 = -6mA$$


$$\frac{12}{1K} + \frac{V_1}{4k} + \frac{V_1 - (-12)}{2k} = 0 \Rightarrow V_2 = -6V$$

$$V_1 = 8V; I_0 = 2mA$$


$$\Rightarrow V_1 = 8V; I_0 = 2mA$$

**Problem 3.24**

Find  $I_0$  in the network shown.

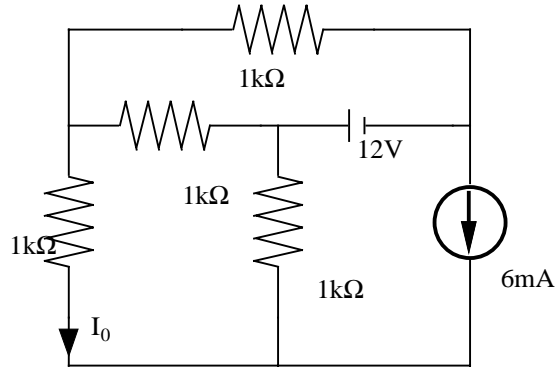

### Suggested Solution

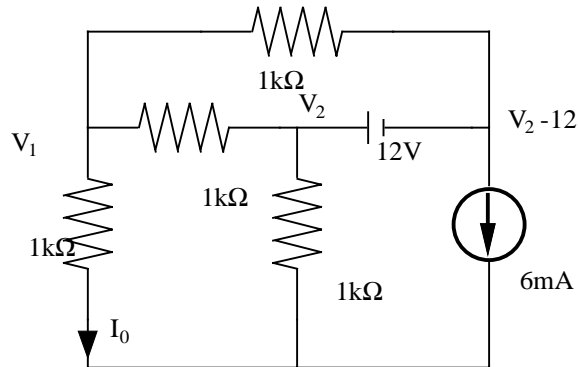

$$\frac{V_1}{1k} + \frac{V_1 - V_2}{1k} + \frac{V_1 - (V_2 - 12)}{1k} = 0$$

$$\frac{V_2 - V_1}{1k} + \frac{V_2}{1k} + \frac{V_2 - 12 - V_1}{1k} + \frac{6}{k} = 0$$

$$\frac{3V_1}{1k} - \frac{2V_2}{1k} = \frac{-12}{1k}; \quad \frac{-2V_1}{1k} + \frac{3V_2}{1k} = \frac{6}{k}$$

⇒

$$3V_1 - 2V_2 = -12$$

$$-2V_1 + 3V_2 = 6$$

⇒


$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 3 & -2 \\ -2 & 3 \end{bmatrix} \begin{bmatrix} -12 \\ 6 \end{bmatrix} = \begin{bmatrix} \frac{-24}{5} \\ \frac{-6}{5} \end{bmatrix}$$

$$I_0 = \frac{V_1}{1k} = \frac{\frac{-24}{5}}{1k} = -4.8mA$$


$$I_0 = -4.8mA$$
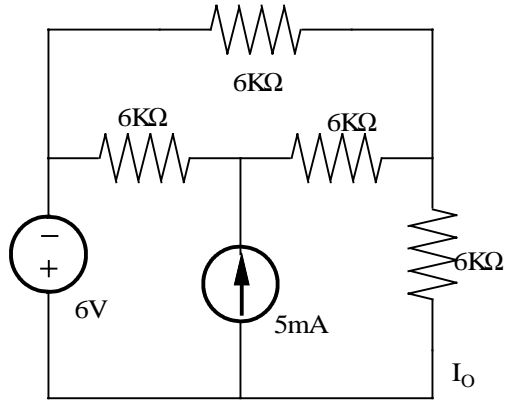
### Problem 3.53

Find  $I_0$  in the network shown using loop analysis. Then solve the problem using matlab and compare your answers.



### Suggested Solution

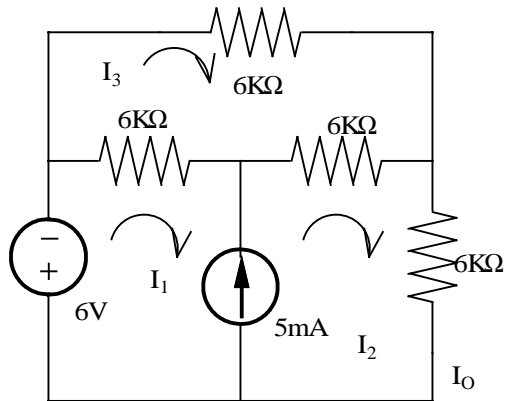

$$6 + 6K(I_1 - I_3) + 6K(I_2 - I_3) + 6KI_2 = 0$$

$$6KI_3 + 6K(I_3 - I_2) + 6K(I_3 - I_1) = 0$$

$$I_2 - I_1 = \frac{5}{K}$$

$$\begin{bmatrix} 6K & 12K & -12K \\ -6K & -6K & 18K \\ -1K & 1K & 0 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} -6 \\ 0 \\ 5 \end{bmatrix}$$

Using Matlab

```
EDU> Z=[6000 12000 -12000;-6000 -6000 18000;-1000 1000 0]
```

Z =

```

6000    12000   -12000
-6000   -6000    18000
-1000    1000     0

```

```
EDU> V=[-6;0;5]
```

V =

-6  
0  
5


EDU»  $I = \text{inv}(Z) * V$

I =

-0.0046  
0.0004  
-0.0014

### Problem 3.70

Find  $V_o$  in the circuit shown.

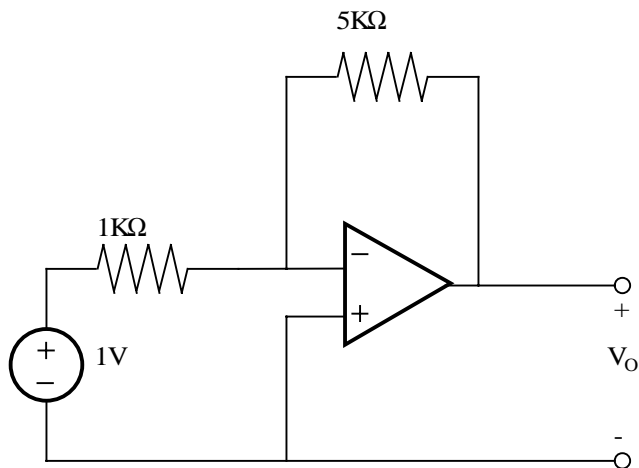

### Suggested Solution


KCL at the intersecting input

$$\frac{1-0}{0.1K} = \frac{0-V_o}{5K}$$
$$V_o = -5V$$

$$V_o = -5V$$
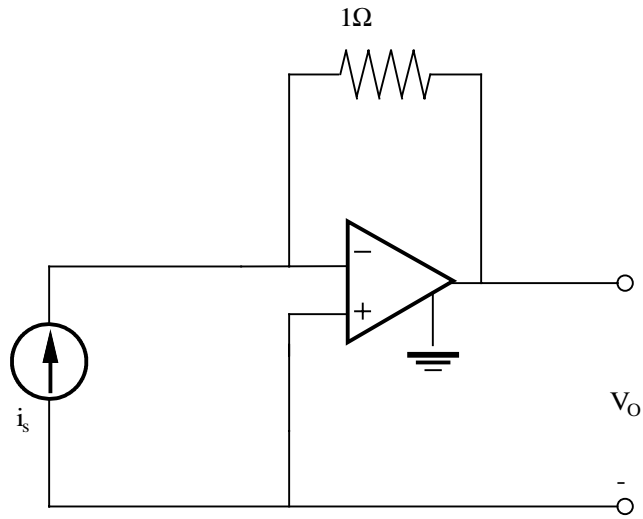
### Problem 3.73

The network shown is a current-to-voltage converter or transresistance amplifier. Find  $V_o/I_s$  for this network.



### Suggested Solution

KCL at the inverting input is

$$\frac{5-4}{1} = \frac{0-V_o}{1}$$

$$\frac{V_o}{i_s} = -1$$

$$\frac{V_o}{i_s} = -1$$