
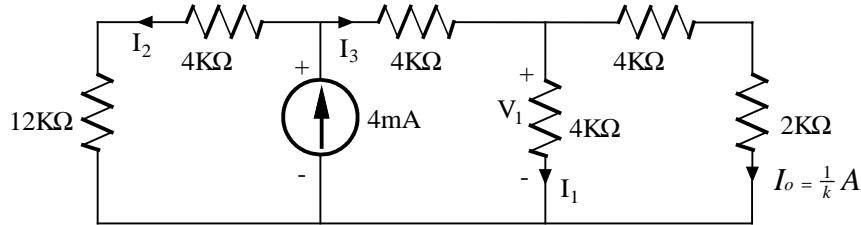


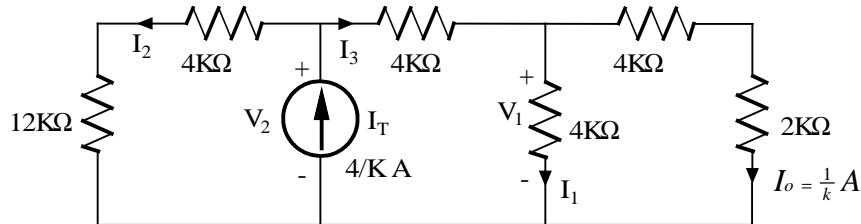Problem 4.1

Find I_o in the circuit shown using linearity and the assumption that $I_o = 1\text{mA}$.



Suggested Solution



If $I_o = \frac{1}{k} A$ Then $V_2 = \frac{1}{k}(4K + 2K) = 6V$, $I_1 = \frac{6}{4k} = \frac{3}{2} mA$


Then $I_2 = I_1 + I_o = \frac{5}{2} mA$ and $V_2 = V_1 + 4KI_2 = 16V$

Then $I_3 = \frac{V_2}{4K + 12K} = 1mA \therefore I_T = I_2 + I_3 = \frac{7}{2} mA$


So $\frac{7/2 mA}{1mA} = \frac{4mA}{x} \therefore x = \boxed{I_o = \frac{8}{7} mA}$

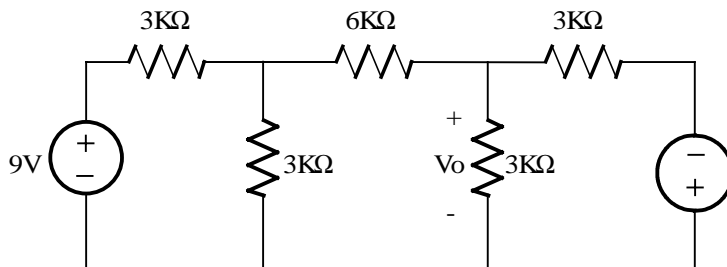Problem 4.8


Find V_o in the network shown using superposition



Suggested Solution

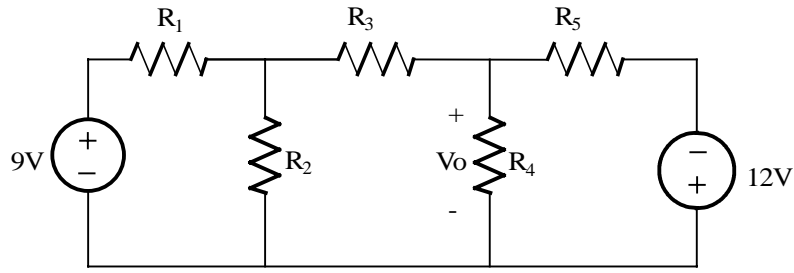


$R_3=6K\Omega$ All other $R=3K\Omega$

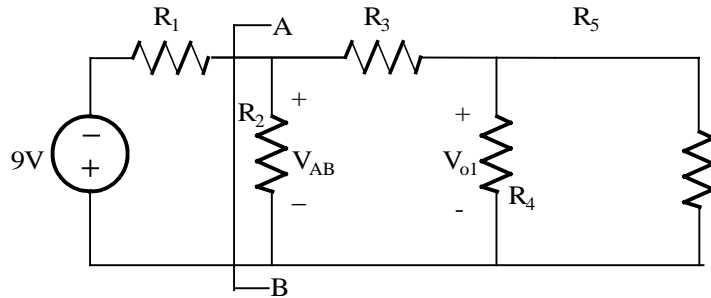

$$R_{AB} = R_2 \parallel [R_3 + (R_4 \parallel R_5)] = 2.14K\Omega$$

$$V_{AB} = 9\left(\frac{R_{AB}}{R_{AB}+R_1}\right) = 3.75V$$
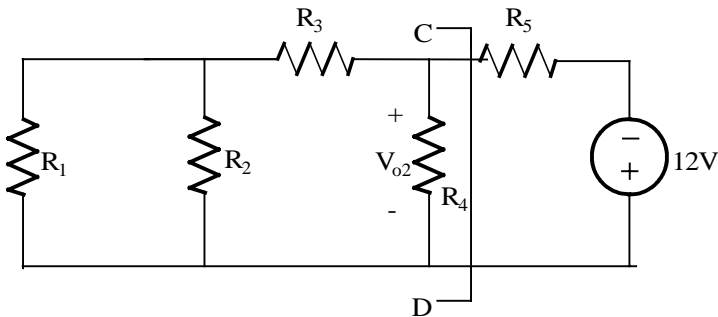
$$V_{o1} = V_{AB}\left(\frac{R_4 \parallel R_5}{(R_4 \parallel R_5)+R_3}\right) = 0.75V$$




$$R_{CD} = R_4 \parallel [R_3 + (R_1 \parallel R_2)] = 2.14K\Omega$$

$$V_{o2} = -12\left(\frac{R_{CD}}{R_{CD}+R_5}\right) = -5V$$






$$V_O = V_{o1} + V_{o2} = -4.25V$$

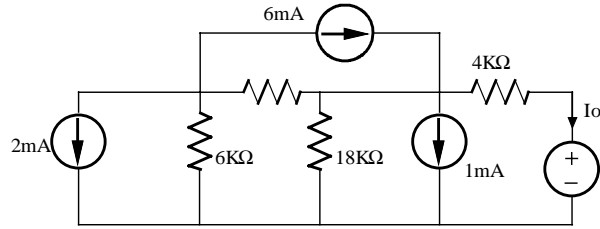Problem 4.24

Find I_o in the network shown using source transformation.




Suggested Solution

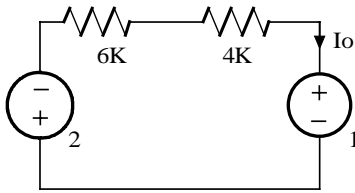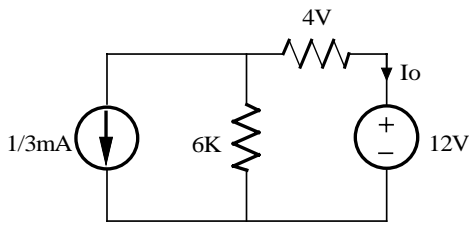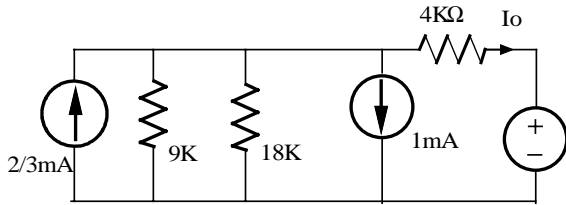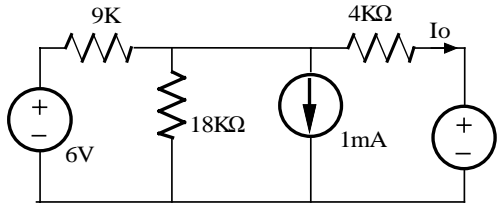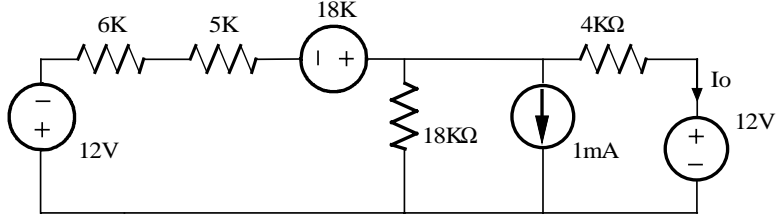


$$I_o = -14/10K = -7/5mA$$

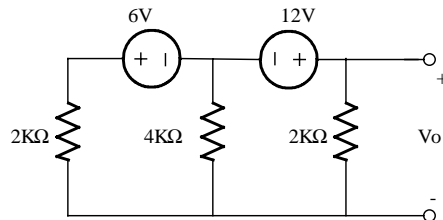Problem 4.33

Use Thevenin's Theorem to find V_o in the network shown.




Suggested Solution

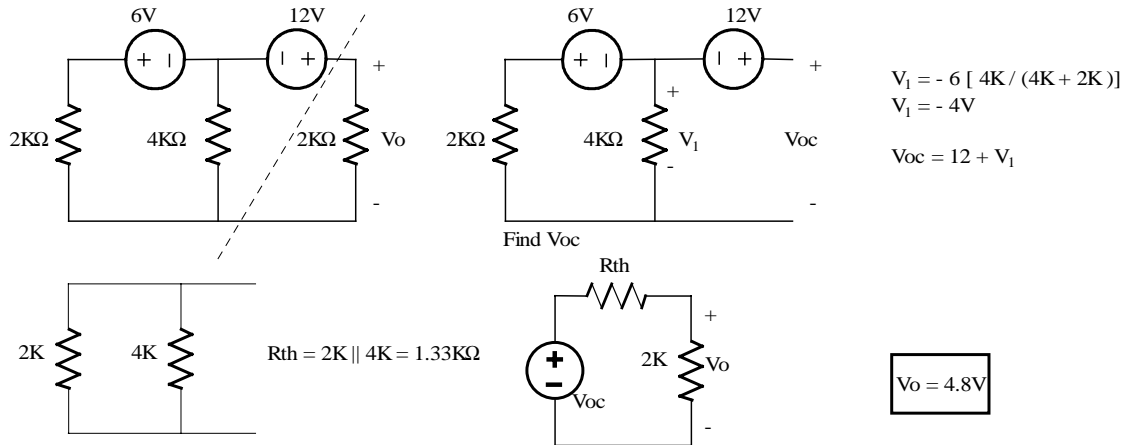


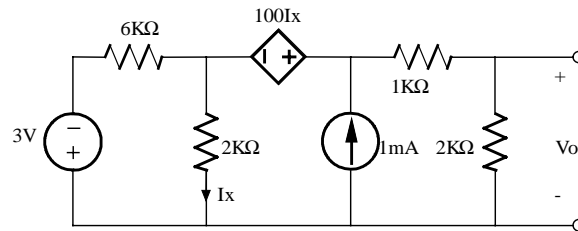Problem 4.58

Find V_o in the network shown using Thevenin's Theorem.



Suggested Solution

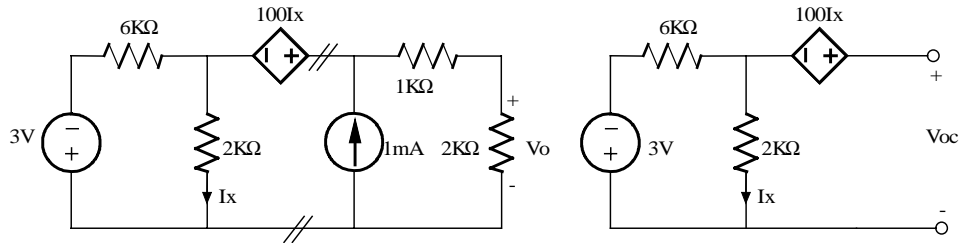


$$I_x = -3/8K = -0.38 \text{ mA}$$

$$3 + (6K)I_x - (1K)I_x + V_{oc} = 0$$

$$V_{oc} = -1.13V$$
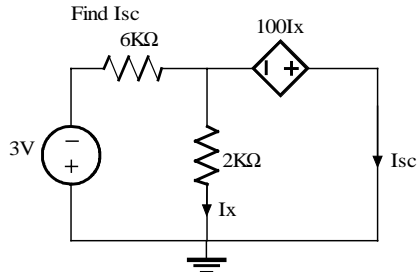
$$R_{th} = V_{oc} / I_{sc} = 2.25 \text{ K}\Omega$$




$$V_x = 2000I_x$$


$$V_x = -1000 I_x$$

$$V_x = 0 \text{ and } I_x = 0A$$
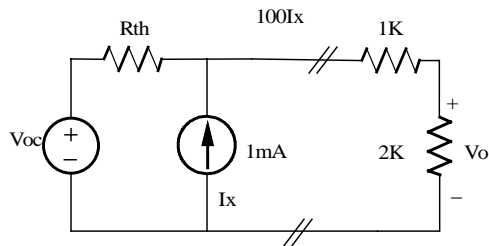
$$\text{Now, } -3/6K = I_{sc} \Rightarrow I_{sc} = -0.5mA$$





$$V_{oc} = -1.13V, R_{th} = 2.25K$$

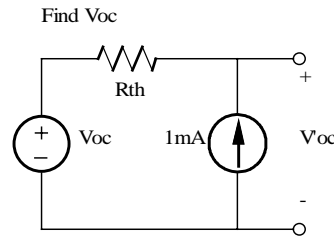

$$V'_{oc} = (1m)R_{th} + V_{oc}$$


$$V_{oc} = 1.13V$$

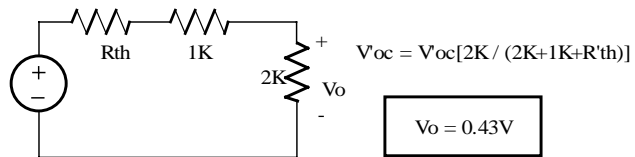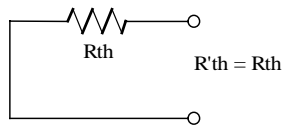



$$V_o = 0.43V$$

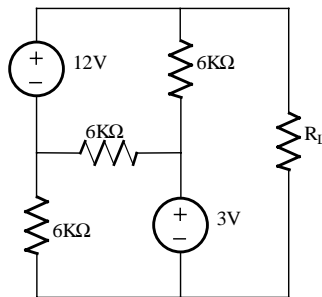Problem 4.70

Find R_L for maximum power transfer and the maximum power that can be transferred in the network shown.



Suggested Solution

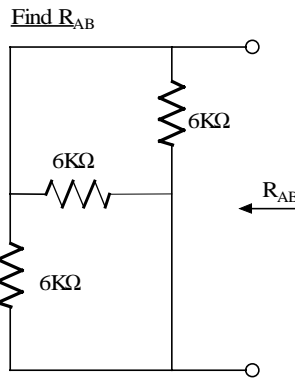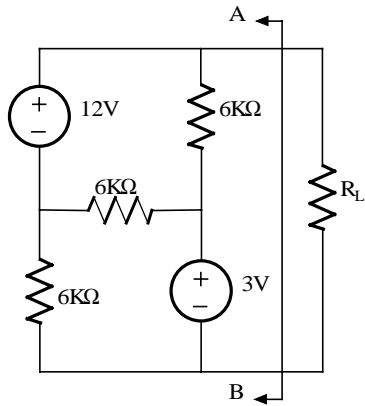


All 3 Resistors are attached to both node A and node B, so,

$$R_{AB} = 6K \parallel 6K \parallel 6K$$

$$R_{AB} = 2K\Omega$$

Find maximum load transfer

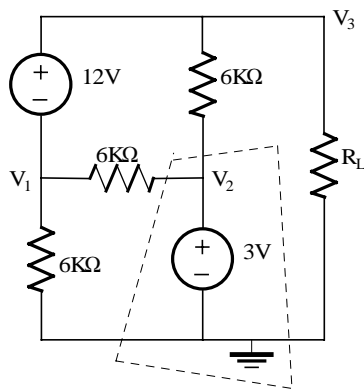

$$V_3 - V_1 = 12V$$

$$V_2 = 3V$$

At supernode:

$$(V_3 - V_2) / 6K + (V_1 - V_2) / 6K + V_3 / 2K + V_1 / 6K = 0$$

Yields:

$$V_3 = 5V$$

$$P_L = V_3^2 / R_{AB}$$

$$P_L = 12.5 \text{ mW}$$