

E245B

HW #6, 10/25/01

Problem 5.64

For the network in Figure P5.64 choose C such that

$$v_o = -10 \int v_s dt$$


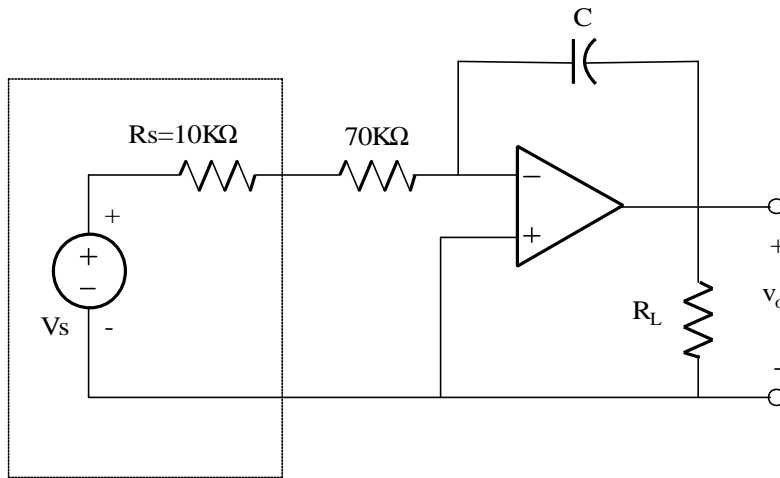


Figure P5.64

Suggested Solution

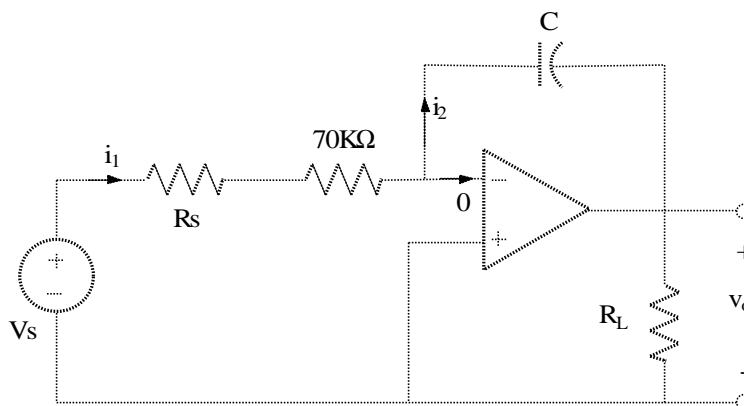

$$R_s = 10K\Omega$$

$$v_o = -10 \int v_s dt$$

$$R_{eq} = R_s + 70K = 80K$$

Using ideal op-amp assumptions,

$$i_1 = i_2$$


$$\frac{v_s - 0}{R_{eq}} = -C \frac{dv_o}{dt} \Rightarrow v_o = -\frac{1}{R_{eq} C} \int v_s dt$$

So,

$$R_{eq} C = \frac{1}{10} \Rightarrow \boxed{C = 1.25mF}$$

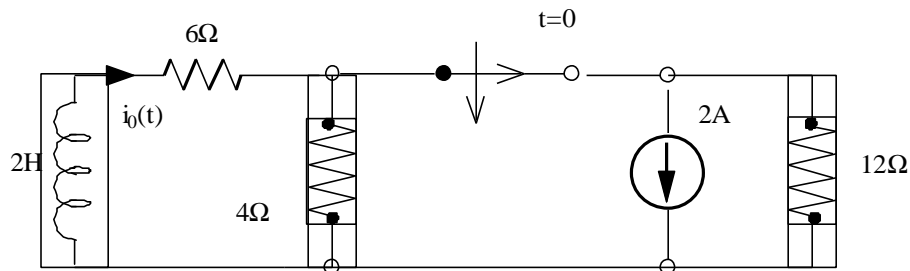Problem 6.5

In the network in Fig P6.5, find $i_o(t)$ for $t > 0$ using the differential equation approach.



Suggested Solution

$$i_L(0^-) = 2 \left(\frac{3}{3+6} \right) = \frac{2}{3} \text{ A} \quad \text{using current division}$$

$$L \frac{di_o(t)}{dt} + 10i_o(t) = 0 \quad 10 = 6 + 4$$


$$\therefore i_o(t) = K_2 e^{-5t} \text{ A} \quad 5 = \frac{10}{L} = \frac{10}{2}$$

$$\text{So, } i_o(0) = \frac{2}{3} = K_2$$


Then, $i_o(t) = \frac{2}{3} e^{-5t}$ A, $t > 0$

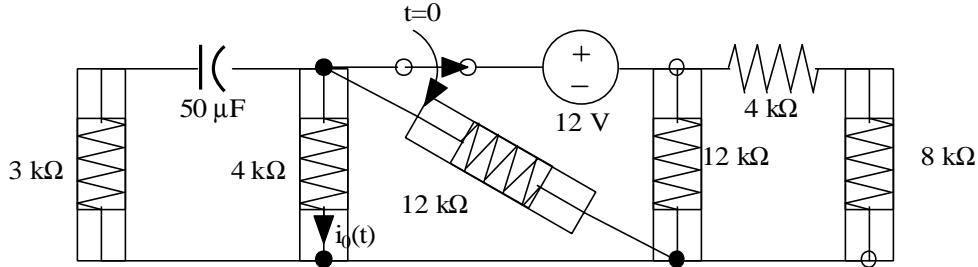Problem 6.21

Use the differential equation approach to find $i_o(t)$ for $t > 0$ in the circuit in Fig. P.21 and plot the response including the time interval just prior opening the switch.



Suggested Solution

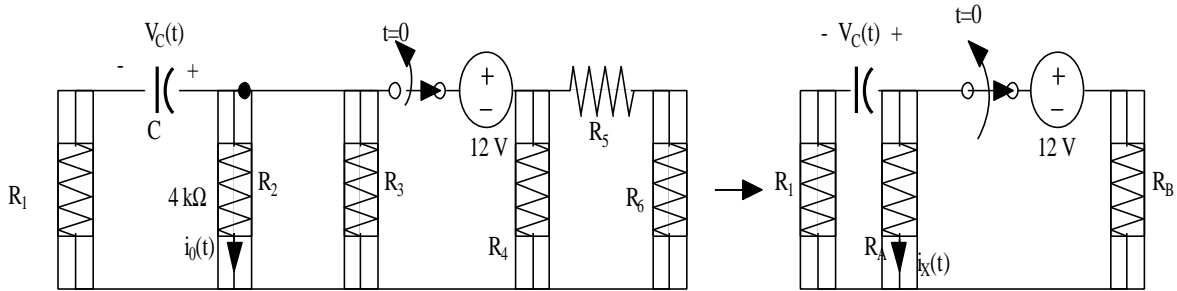


$R_1 = 3 \text{ k}\Omega$ $R_2 = R_5 = 4 \text{ k}\Omega$ $R_3 = R_4 = 12 \text{ k}\Omega$ $R_6 = 8 \text{ k}\Omega$ $C = 0.05 \text{ mF}$ $R_A = 3 \text{ k}\Omega$ $R_B = 6 \text{ k}\Omega$

For $t < 0$: $V_c(t) = \frac{-12R_A}{(R_A + R_B)} = -4 \text{ V} = V_c(0^-) = V_c(0^+)$

$i_x(0^-) = \frac{V_c(0^-)}{R_A} = \frac{-4}{3} \text{ mA}$ $i_o(0^-) = \frac{i_x(0^-)R_3}{(R_2 + R_3)} = -1 \text{ mA}$

For $t > 0$: By KCL: $\frac{C}{dt} \frac{dV_c(t)}{dt} + \frac{V_c(t)}{R_1 + R_A} = 0 \Rightarrow \frac{dV_c}{dt} + \frac{10}{3} = 0$

For $t > 0$

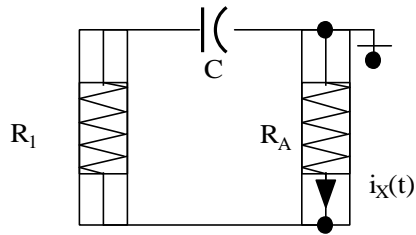


If $V_C(t) = K_1 + K_2 e^{-\frac{t}{\tau}}$, then $\tau = 0.3 \text{ s}$ and $K_1 = 0$

$$V_C(0^+) = K_2 = -4\text{V} \text{ so, } V_C(t) = -4e^{-\frac{10t}{3}} \text{ V}$$


$$\text{But } i_X(t) = \frac{-V_C(t)}{R_1 + R_A} \text{ and } i_0(t) = \frac{i_X(t)R_3}{R_2 + R_3} \Rightarrow \begin{cases} i_0(t) = 0.5e^{-\frac{10t}{3}} \text{ mA, } t > 0 \\ = 1 \text{ mA, } t < 0 \end{cases}$$

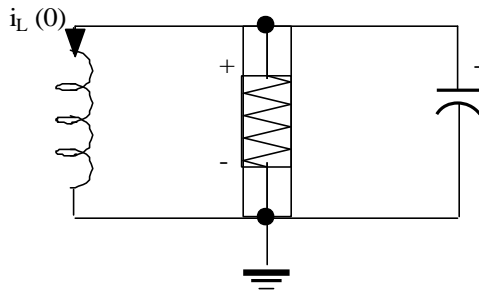Problem 6.61

For the underdamped circuit shown in Fig. 6.61 determine the voltage $v(t)$ if the initial conditions on the storage elements are $i_L(0) = 1 \text{ A}$ and $v(0) = 10 \text{ V}$.



Suggested Solution

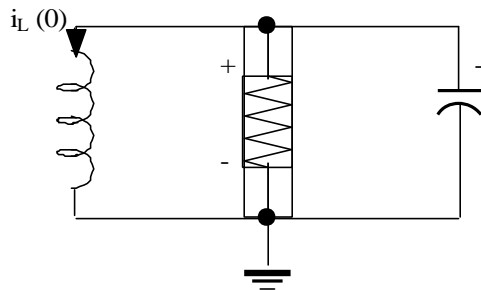

Find $V(t)$ if $i_L(0)=1A$ and $v_c(0)=10v$

$$\frac{d^2v(t)}{dt^2} + \frac{1}{RC} \frac{dv(t)}{dt} + \frac{1}{LC} v(t) = 0$$

The characteristic equation is

$$s^2 + 8s + 20 = 0$$

$$s = -4 \pm 2j$$

so

$$v(t) = k_1 e^{-4t} \cos 2t + k_2 e^{-4t} \sin 2t$$

at

$$t = 0, v_c = 10$$

$$v(t) = k_1 = 10$$

then

$$\frac{dv(t)}{dt} = -2k_1 e^{-4t} \sin 2t - 4k_1 e^{-4t} \cos 2t + 2k_2 e^{-4t} \cos 2t - 4k_2 e^{-4t} \sin 2t$$

at

$$t = 0$$

$$\frac{dv(t)}{dt} = -4k_1 + 2k_2 = -40 + 2k_2$$

also

$$\frac{cdv(t)}{dt} + \frac{v(t)}{R} + i_L(t) = 0$$

at

$$t = 0$$

$$\frac{dv(t)}{dt} = \frac{1}{c} \left(\frac{-v(t)}{R} - i_L(t) \right) = \frac{1}{c} \left(\frac{-10}{R} - 1 \right)$$

if


$$-40 + 2k_2 = -120$$

finally


$$v(t) = 10e^{-4t} \cos 2t - 40e^{-4t} \sin 2t$$

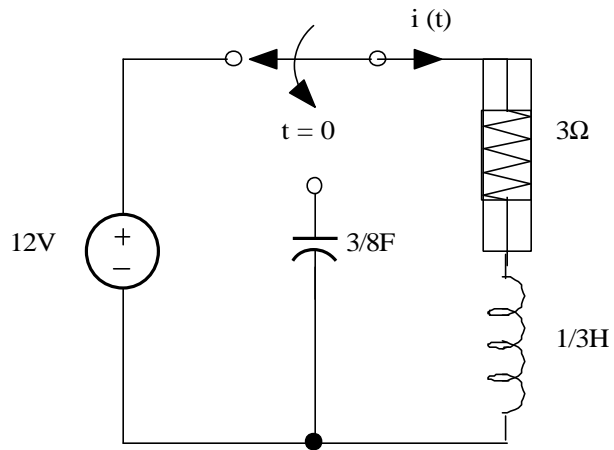Problem 6.67

Given the circuit in Fig. 6.67, find the equation for $i(t)$, $t > 0$.



Suggested Solution

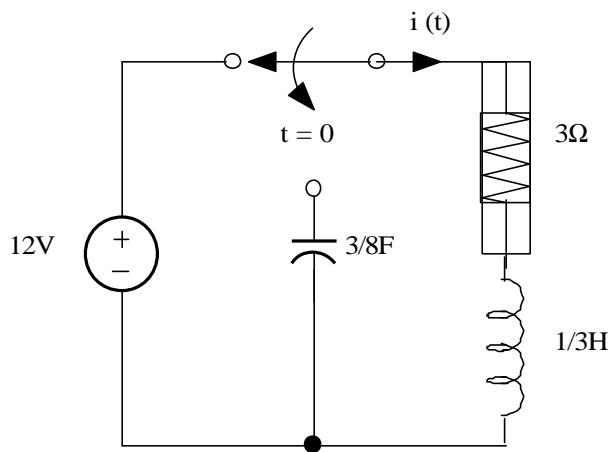

for

$$t < 0$$

$$i_L = 12/3 = 4A, v_c = 0V$$

for

$$t = 0^+$$

$$i_L = 4A, v_c = 0V$$

for

$$t > 0$$

Series RLC circuit

$$s^2 + \frac{R}{L}s + \frac{1}{LC} = 0 \Rightarrow s^2 + 9s + s = 0 \Rightarrow (s+8)(s+9) = 0$$

since roots are real and unequal, overdamped and

$$i(t) = k_1 e^{-t} + k_2 e^{-8t}$$

$$i(0) = 4 = k_1 + k_2$$

KCL:

$$v_c(0^+) = Ri(0^+) + L \left. \frac{di(t)}{dt} \right|_{t=0} \Rightarrow 0 = 12 + \frac{1}{3}(-k_1 - 3k_2)$$

so

$$k_1 + k_2 = 4$$

$$k_1 + 8k_2 = 36$$

$$k_1 = \frac{-4}{7}, k_2 = \frac{32}{7}$$

$$i(t) = \frac{32}{7} e^{-8t} - \frac{4}{7} e^{-t} A \quad \text{for } t > 0$$