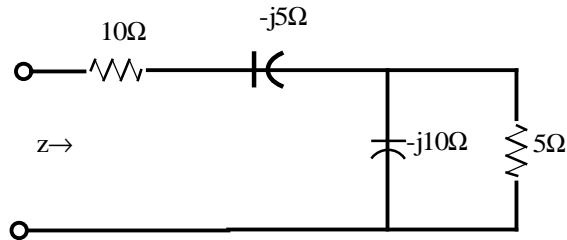


E245B

HW #7 solns., 11/08/01

Problem 7.12

Find the frequency domain impedance, Z , for the network shown.



Suggested Solution

$$Z = 10 - 5j + \frac{5(-10j)}{5 - 10j} = 10 - 5j + \frac{5(-10j)}{11.2 \angle -23.4^\circ} = 10 - 5j + 4 - 2j = 14 - 7j = 15.65 \angle -26.6^\circ \Omega$$

Problem 7.22

The voltages $v_R(t)$, $v_L(t)$, and $v_C(t)$ in the circuit shown can be drawn as phasors in a phasor diagram. Show that $v_R(t) + v_L(t) + v_C(t) = v_S(t)$.

Suggested Solution

$$V_R(t) = i(t)R = 2(4.37) \cos(377t + 0.75^\circ) = 8.74 \cos(377t + 0.75^\circ) V$$


$$V_R = 8.74 \angle 0.75^\circ V$$

$$V_L(t) = L \frac{di}{dt} = (10^{-2})(4.37)(377)(-\sin(377t + 0.75^\circ)) = 16.47 \cos(377t + 90.75^\circ)$$

$$V_L = 16.47 \angle 90.75^\circ V$$


$$V_C(t) = \frac{1}{C} \int i dt = \left(\frac{1}{10^{-3}} \right) \left(\frac{1}{377} \right) (4.37) \sin(377t + 0.75^\circ)$$

$$V_C(t) = 11.59 \cos(377t - 89.25^\circ) V$$

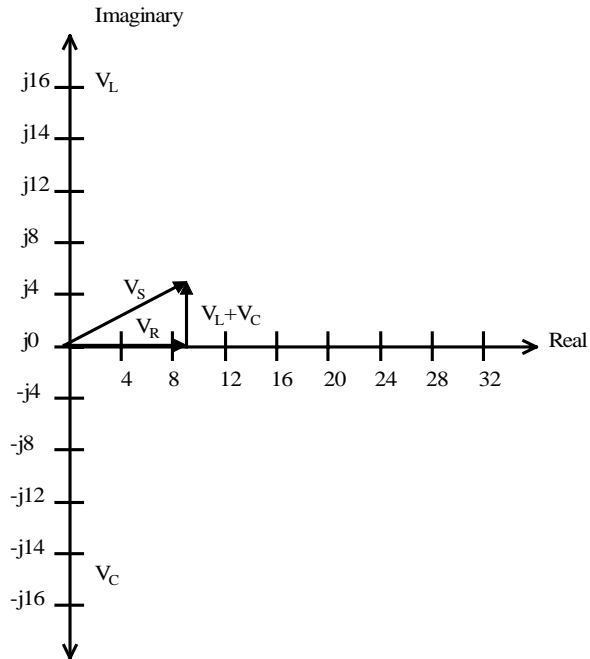

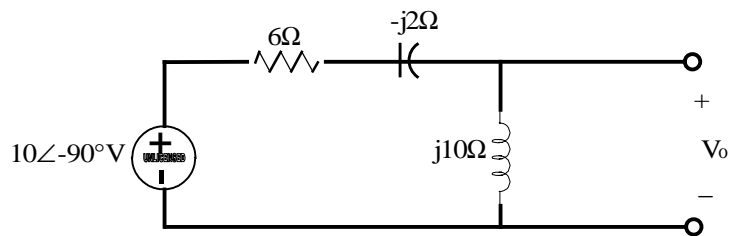Problem 7.28

Find the frequency domain voltage V_0 as shown.



Suggested Solution

$$V_0 = 10 \angle -90^\circ \frac{10j}{6 - 3j + 10j} = \frac{(10 \angle -90^\circ)(10 \angle 90^\circ)}{10 \angle 53^\circ} = 10 \angle -53.1^\circ \text{ V}$$