

# E245B

## HW #8 solns., 11/28/01

### Problem 9.13

Calculate the average power absorbed by the 1-Ω resistor in the network shown in Fig. P 9.13


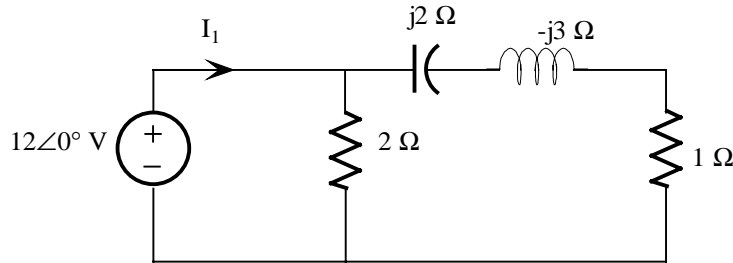


Figure P9.13

### Suggested Solution

#### Theremin's Equation

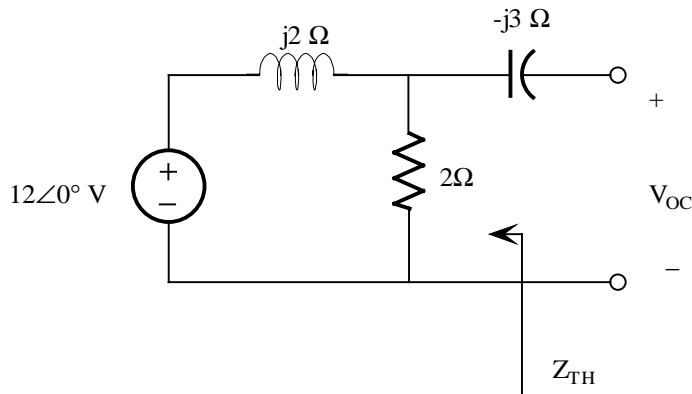


$$V_{oc} = 12 \angle 0^\circ \left[ \frac{2}{2 + j2} \right]$$

$$V_{oc} = \frac{24 \angle 0^\circ}{2\sqrt{2} \angle 45^\circ} \quad V_{oc} = 8.49 \angle -45^\circ \text{ V}$$

$$Z_{TH} = -j3 + (2 \parallel j2)$$

$$Z_{TH} = -j3 + \frac{j4}{2 + j2} = -j3 + \frac{4 \angle 90^\circ}{2\sqrt{2} \angle 45^\circ} = -j3 + \sqrt{2} \angle 45^\circ = -j3 + 1 - j1$$

$$Z_{TH} = (1 - j2) \Omega$$

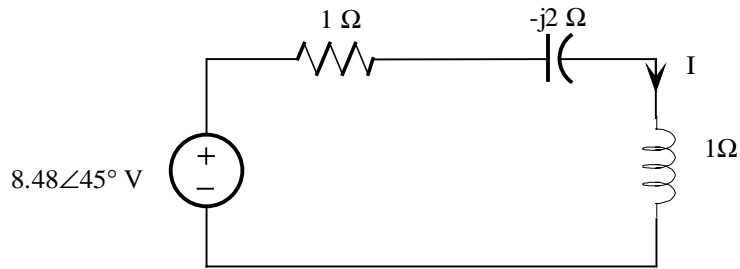

$$P_R = I^2 R / 2$$

$$I = \frac{8.49 \angle -45^\circ}{2 - j2} = \frac{8.49 \angle -45^\circ}{2\sqrt{2} \angle -45^\circ} = 3 \angle 0^\circ \text{ A}$$

$$P_R = \frac{1}{2} I^2 R = \left(\frac{1}{2}\right)(3)^2(1) = \boxed{4.5 \text{ W}}$$

Problem 9.26

Repeat problem 9.24 for the network in Fig P 9.27



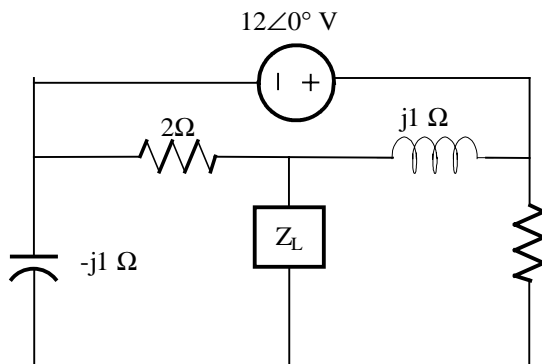


Figure 9.26

Suggested Solution

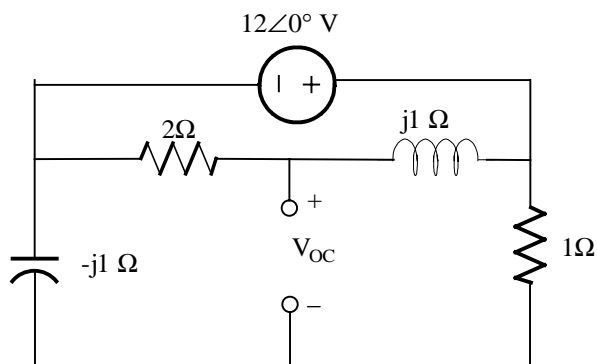
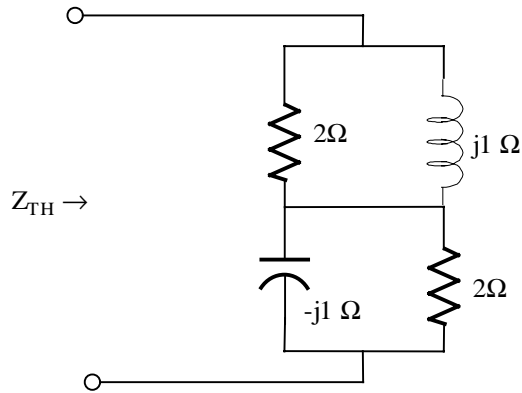
$$V_{OC} = \frac{12 \angle 0^\circ}{2 + j} (2) - \frac{12 \angle 0^\circ}{1 - j} (-j) = 3.79 \angle 18.43^\circ \text{ V}$$



$$Z_{TH} = \frac{2j}{2+j} + \frac{-j}{1-j}$$

$$= \frac{3}{3-j} = .9 + j.3\Omega$$

$$\therefore Z_L = .9 - j.3\Omega$$

$$P_L = \frac{1}{2} \left( \frac{3.79}{1.8} \right)^2 (.9) = 2W$$

### Problem 9.37

Calculate the rms value of the waveform shown in Fig P 9.37

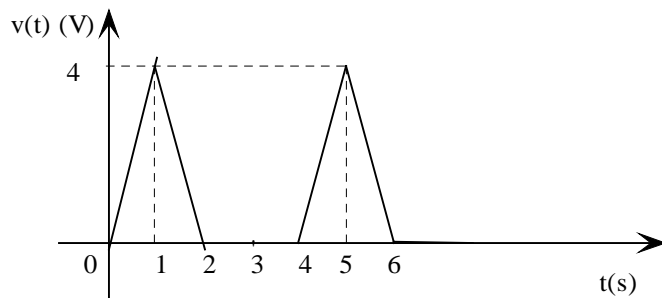


Figure P 9.37

### Suggested Solution

$$I_{rms} = \sqrt{\frac{1}{4} \left[ \int_0^1 (4t)^2 dt + \int_1^2 (8-4t)^2 dt \right]}$$

$$= \sqrt{\frac{1}{4} \left( \frac{16}{3} + \left( 64t - \frac{64t^2}{2} + \frac{16t^3}{3} \right) \Big|_1^2 \right)} = \boxed{1.63V}$$

### Problem 9.51

Given the network in Fig P 9.51, compute the input source voltage and the input power factor.

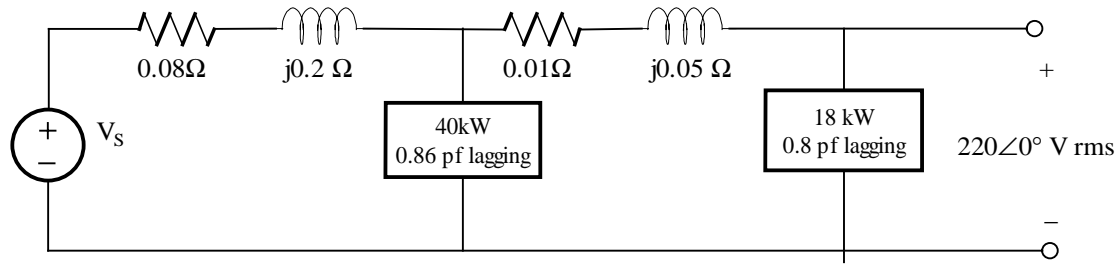


Figure P 9.51

### Suggested Solution

$$\theta_L = \cos^{-1} .8 = 36.87^\circ$$

$$I_{L_2} = \frac{80000}{(220)(.8)} = 102.27 A$$

$$I_{L_2} = 102.27 \angle -36.87^\circ A$$

$$V_{L_1} = (.01 + j.05)(102.27 \angle -36.87^\circ) + 220 \angle 0^\circ$$

$$= 223.91 \angle .89^\circ V$$

$$\theta_1 = \cos^{-1} .86 = 30.68^\circ \text{lagging}$$

$$I_{L_1} = \frac{40000}{(223.91)(.86)} = 207.72 A$$

$$I_{L_1} = 207.72 \angle (-30.68^\circ + .89^\circ) = 207.72 \angle -29.79^\circ A$$

$$I_L = I_{L_1} + I_{L_2} = 207.72 \angle -29.79^\circ + 102.27 \angle -36.87^\circ A$$

$$= 309.47 \angle -32.12^\circ A$$

$$V_S = (309.47 \angle -32.12^\circ)(.08 + j.2) + 223.91 \angle .89^\circ$$

$$= 281.02 \angle 8.75^\circ V$$

$$\theta_S = \theta_{V_S} - \theta_{I_S} = 8.75^\circ - (-32.12^\circ) = 40.87^\circ$$

$$P_{\text{Source}} = \cos(40.87^\circ) = \boxed{.756 \text{lagging}}$$

$$\theta_L = \cos^{-1}.8 = 36.87^\circ$$

$$I_{L_2} = \frac{80000}{(220)(.8)} = 102.27 A$$

$$I_{L_2} = 102.27 \angle -36.87^\circ A$$

$$V_{L_1} = (.01 + j.05)(102.27 \angle -36.87^\circ) + 220 \angle 0^\circ$$

$$= 223.91 \angle .89^\circ V$$

$$\theta_1 = \cos^{-1}.86 = 30.68^\circ \text{lagging}$$

$$I_{L_1} = \frac{40000}{(223.91)(.86)} = 207.72 A$$

$$I_{L_1} = 207.72 \angle (-30.68^\circ + .89^\circ) = 207.72 \angle -29.79^\circ A$$

$$I_L = I_{L_1} + I_{L_2} = 207.72 \angle -29.79^\circ + 102.27 \angle -36.87^\circ A$$

$$= 309.47 \angle -32.12^\circ A$$

$$V_S = (309.47 \angle -32.12^\circ)(.08 + j.2) + 223.91 \angle .89^\circ$$


$$= 281.02 \angle 8.75^\circ V$$

$$\theta_S = \theta_{V_S} - \theta_{I_S} = 8.75^\circ - (-32.12^\circ) = 40.87^\circ$$


$$P_{\text{Source}} = \cos(40.87^\circ) = \boxed{.756 \text{lagging}}$$
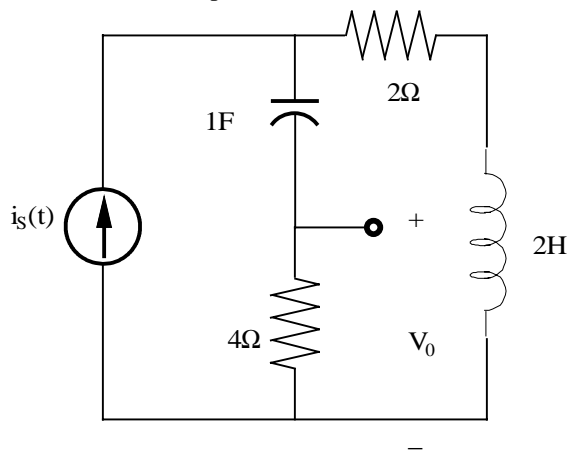
### Problem 11.4

Find the transfer impedance  $V_o(s)/I_s(s)$  for the network shown in fig 11.4.



Suggested Solution

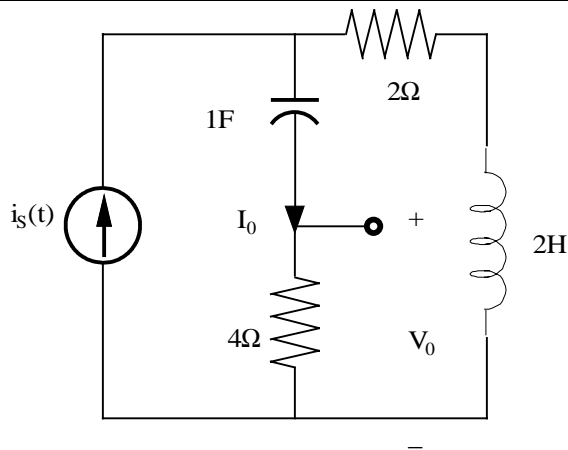

$$I_o = I_s \left[ \frac{2S + 2}{2S + 2 + 4 + \frac{1}{S}} \right]$$

$$\frac{I_o}{I_s} = \frac{2S^2 + 2S}{2S^2 + 6S + 1}, V_o = 4I_o, SO \quad \frac{V_o}{I_s} = \frac{8S(S + 1)}{2S^2 + 6S + 1}$$

$$\frac{8S(S + 1)}{2S^2 + 6S + 1}$$

Problem 11.6

Draw the bode plot for the network function.

Suggested Solution

$$H(j\omega) = \frac{j\omega 5 + 1}{j\omega 20 + 1}$$